



UNIVERSITY OF RWANDA
COLLEGE OF SCIENCE & TECHNOLOGY
SCHOOL OF ENGINEERING
DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

DR. KIZITO NKURIKIYEYEU

EPE 2165—ANALOG ELECTRONICS

HOMEWORK #2—Signals and amplifiers

Question:	1	2	3	4	5	Total
Points:	20	10	10	20	40	100
Score:						

Issued on:

June 23, 2022

Due on:

June 30, 2022

1. **Figure 1** represents a portion of battery-charger circuit for a battery with a voltage V_B . The sine-wave input $v_S = 12\text{ V}(rms)$, while the battery voltage varies from 12 V to 14 V from the discharged to fully charged states. The charging-source resistance $R_S = 10\ \Omega$. Assuming that D is an ideal diode, and $R_C = 50\ \Omega$ is a current-controlling resistor established by the designer:

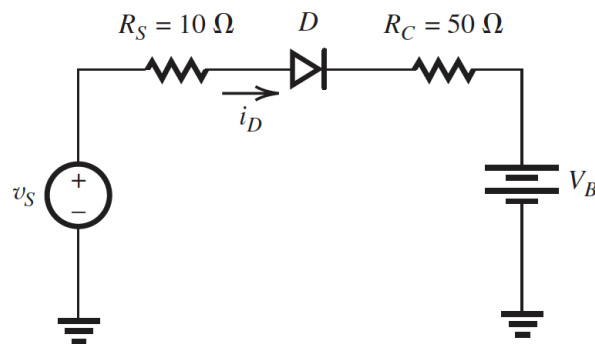


FIGURE 1. Battery-charger circuit

- (a) (10 points) Sketch and label the voltage waveforms of the voltage across the diode and the current through the diode for $V_B = 12\text{ V}$.
 - (b) (10 points) What is the peak diode current?
2. (10 points) For the circuits shown in **Figure 2**, using ideal diodes, find the values the output voltage V_O and the currents I_{D1} and I_{D2} .
 3. (10 points) The diode in the circuit shown in **Figure 3** has a reverse-saturation current of $I_s = 5 \times 10^{-11}\text{ A}$. Determine the diode voltage V_D and current I_D .

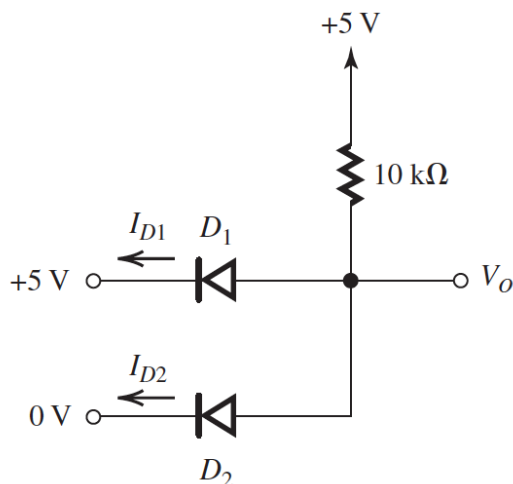


FIGURE 2

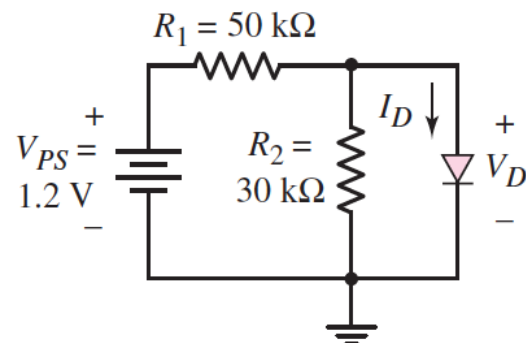


FIGURE 3

4. (20 points) **Figure 4** shows a 4 diode circuit. The 4 diodes are identical and each diode exhibits a voltage drop of $V_D = 0.7V$ at a 1 mA current. For small input signals (e.g., 10-mV peak), find the small-signal equivalent circuit and use it to determine values of the small-signal transmission v_o/v_i for a current $I = 1 \mu A$
5. Consider a half-wave rectifier circuit shown in **Figure 5**.

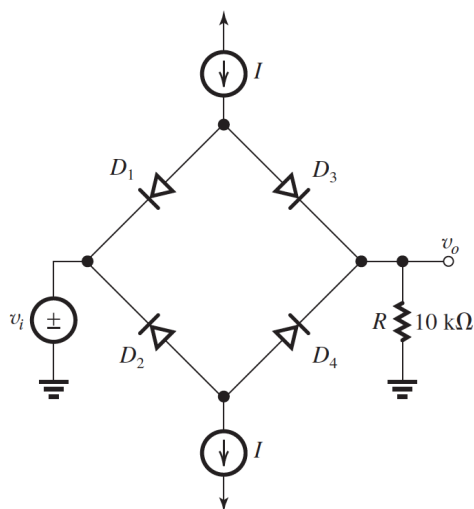


FIGURE 4

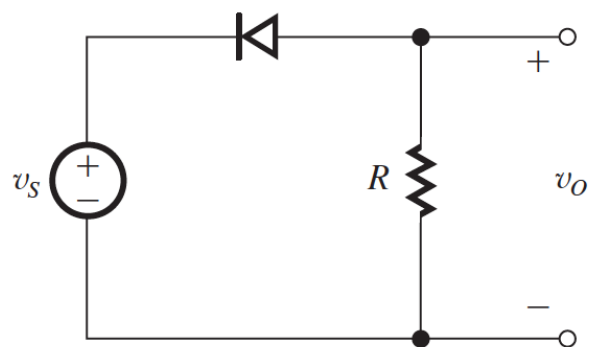


FIGURE 5

Let v_s be a sinusoid with 10V peak amplitude, and let $R = 1k$. Use the constant-voltage-drop diode model with $V_D = 0.7V$.

- (10 points) Sketch the transfer characteristic.
- (10 points) Sketch the waveform of v_o .
- (10 points) Find the peak current in the diode.
- (10 points) Find the PIV of the diode